

CDL Presents Basic Electronics

1

Joe Wilkes, PhD
WA2SFF

June 2025

Joe's Background

2

- Licensed since 1961
 - Extra Class - WA2SFF
- Electrical Engineer
- Co-author of three books on Wireless Communications

June 2025

Outline

3

- Week 1
 - DC circuits
 - Basic formulas
 - AC circuits
 - Basic Parts
- Week 2:
 - Diodes
 - Transistors
- Week 3:
 - Analog Integrated Circuits
- Week 4:
 - Digital Integrated Circuits

June 2025

Week 1

4

Basic Circuits and Formulas

June 2025

DC circuits



5

- Voltage
- Resistors
- Current
- Power
- Ohms Law
- Series and Parallel circuits

June 2025

Direct Current (DC)

- DC means that the current flows in the same direction at all times
- The current can vary with time but is always the same direction
- Current flows from a negative terminal to a positive terminal
- The current flow is electrons moving through a wire or other device that conducts electricity

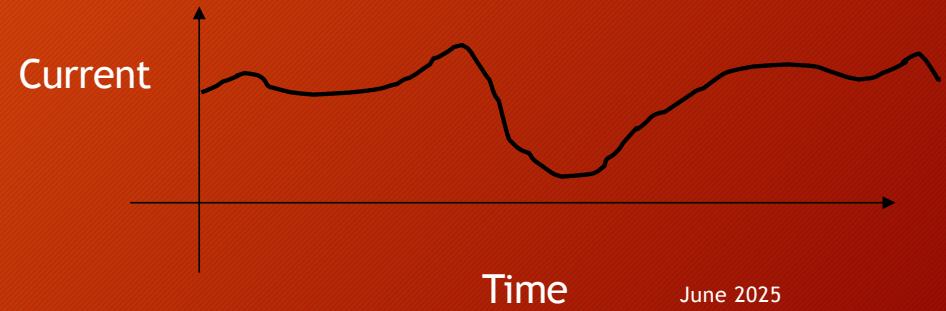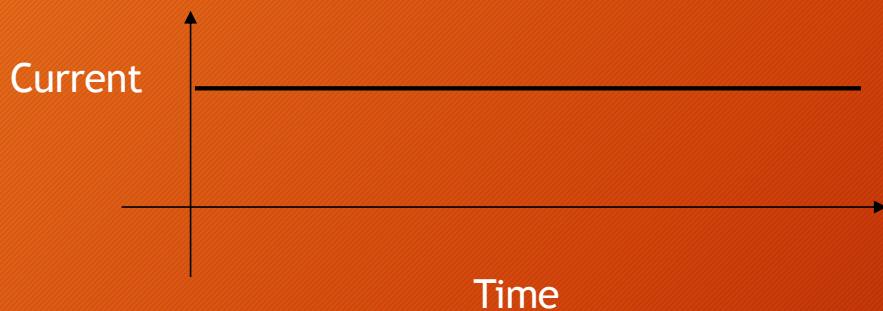

June 2025


Definitions

- The Voltage (V - Volts) is a measure of the strength of an electrical signal
- The Amperage/Current (I, i - Amps) is a measure of the flow of the electrical signal
- A Resistor (R - Ohms) regulates the current for a specified Voltage
- Power (P - Watts) is the heating effect of current flowing through a resistor
- Ohms Law: $V = I \times R$, or $I = V/R$, or $R = V/I$
- $P = I \times I \times R = (I^2 \times R)$

Simple DC Circuit

8

Battery

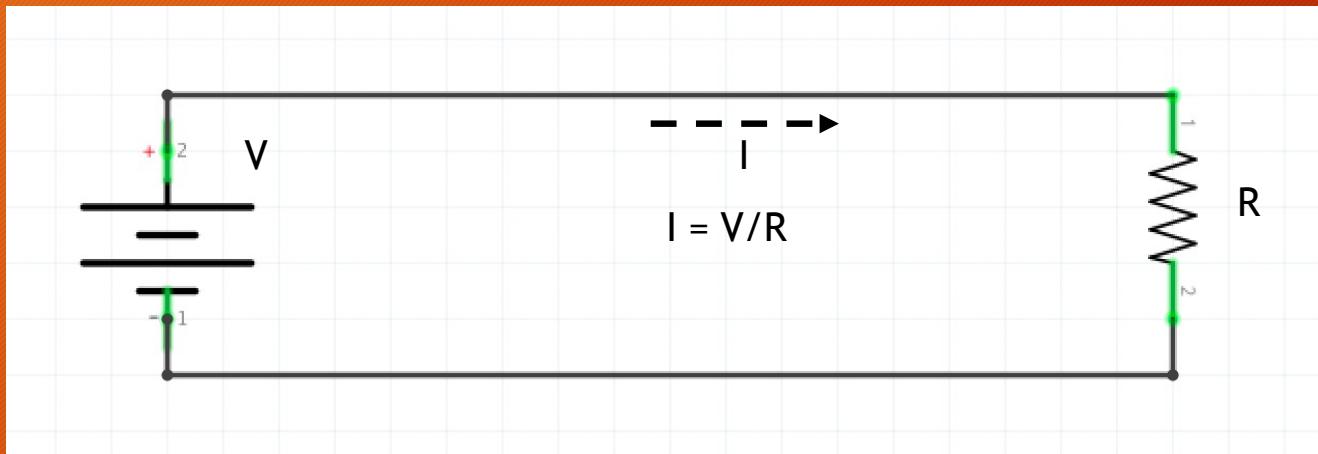

Resistor

June 2025

Resistor Types

- Most electronic resistors are made with carbon with sizes of:
 - 1/8 watt
 - 1/4 Watt
 - 1/2 Watt
 - 1 Watt
 - 2 Watts
- Old radio circuits used carbon resistors
- Newer resistors are metal film and often cause problems in radio circuits
- Try to find "old" carbon resistors when working with old radios
- Larger resistors are often made with wire
- Resistors can be a fixed or variable (adjustable) resistance

Resistors Come in Many Different Forms




Resistor Color Code

- Value:
- 0 Black
- 1 Brown
- 2 Red
- 3 Orange
- 4 Yellow
- 5 Green
- 6 Blue
- 7 Violet
- 8 Grey
- 9 White
- Tolerance
- 1 % Brown
- 5 % Gold
- 10 % Silver
- 20 % nothing

There are various ditties for remembering the color code

Find your favorite using a search engine

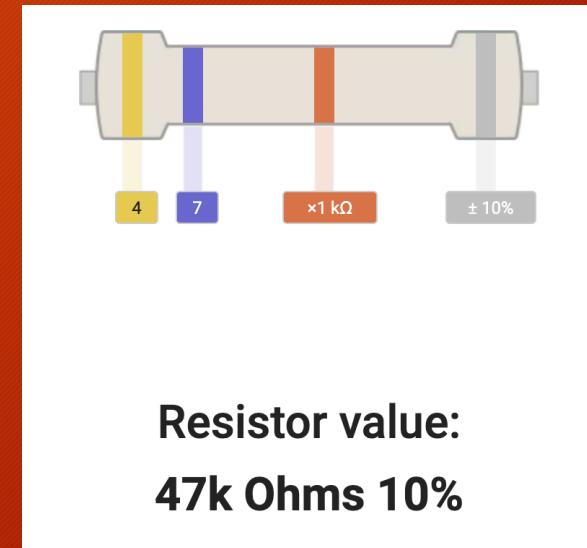


**Resistor value:
47k Ohms 10%**

<https://www.digikey.com/en/resources/conversion-calculators/conversion-calculator-resistor-color-code>

Series and Parallel Circuits

12

Series Circuit

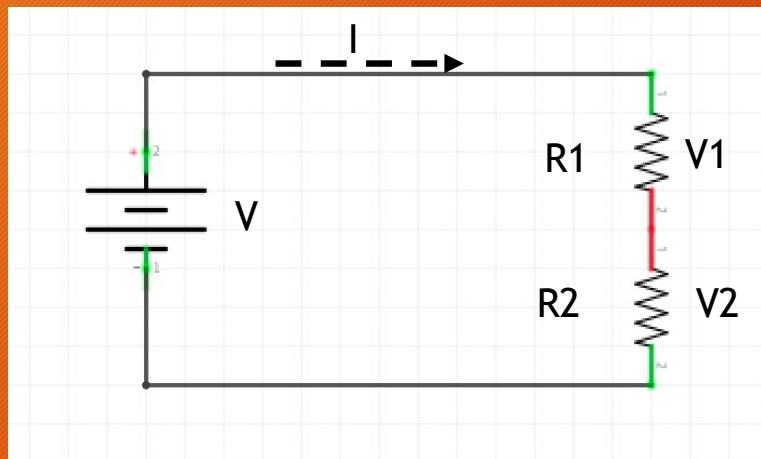


$$I = V / (R_1 + R_2)$$

$$V_1 = \frac{V \times R_1}{R_1 + R_2}$$

$$V_2 = \frac{V \times R_2}{R_1 + R_2}$$

Equivalent Resistance = $R_1 + R_2$

Parallel Circuit

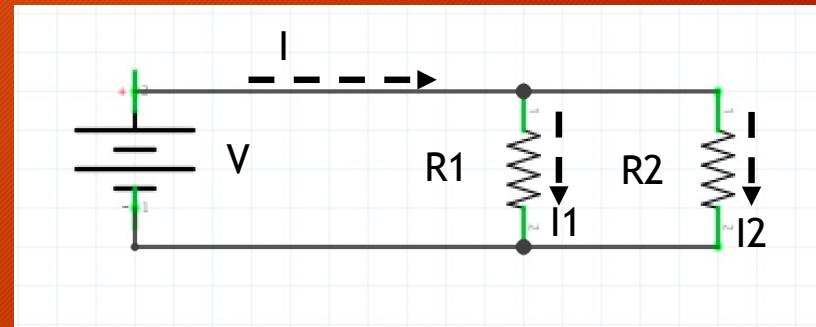

$$I_1 = \frac{V}{R_1} \quad I_2 = \frac{V}{R_2} \quad I = I_1 + I_2$$

$$\text{Equivalent Resistance} = \frac{R_1 \times R_2}{R_1 + R_2}$$

June 2025

How do we measure Voltage and Current?

- We measure with a:
 - Volt Ohm Meter (VOM), or
 - Multimeter
- It measures
 - Volts
 - Amps
 - Ohms
 - Sometime other things



June 2025

AC circuits

14

- Frequency
- Capacitors
- Inductors
- Power Factor
- Resonance
- Q

June 2025


Alternating Current (AC)

15

- In AC, the current flow can reverse direction with time
- Typical AC from your Electric Outlet is in the shape of a sine wave
- AC is measured by frequency (f): how many times per second it reverses direction:
 - originally measured in cycles per second (CPS), now measured in Hertz (Hz)
- In the US, power is delivered at 60 Hz
- In other parts of the world power is delivered at 50 Hz
- With AC we use the word Impedance (Z) to current flow instead of resistance

We use an Oscilloscope to look at AC signals

16

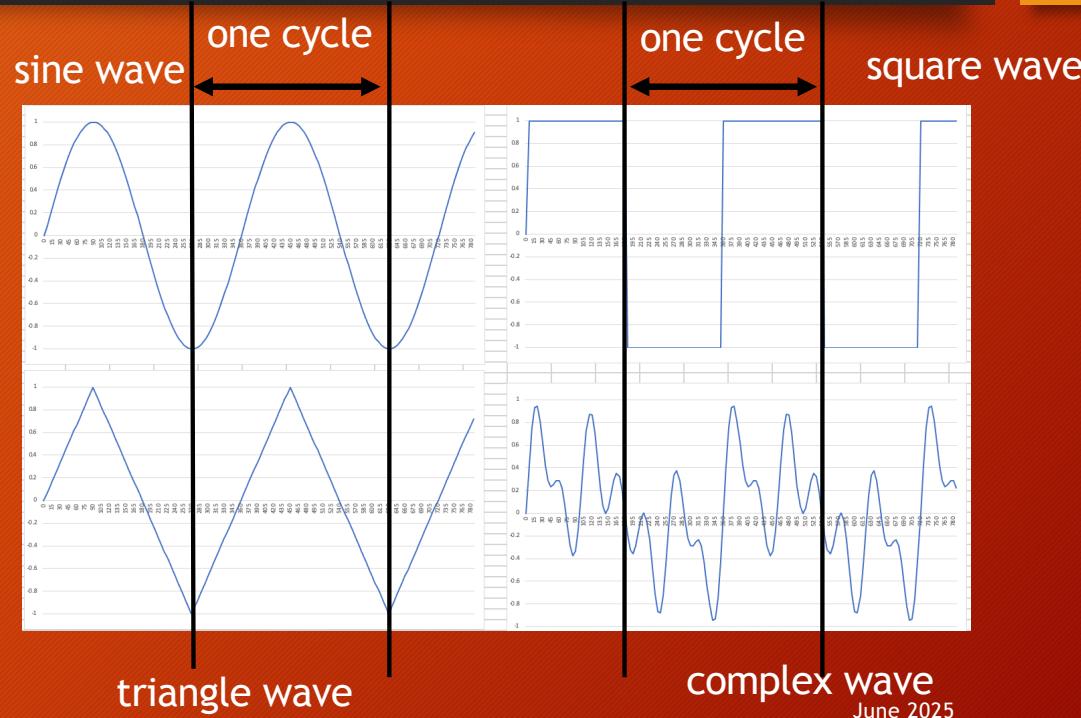

Capacitor


17

- A capacitor (C) passes AC signals and blocks DC signals
- How well a capacitor passes AC signals depends on its value and the frequency of the signal
- A capacitor's values is measured in Farads
- Values range from:
 - micro-micro (pico) Farads (radio circuits) to
 - micro Farads (for audio and power circuits)
 - More recently capacitors with values in the Farad Range are used for very High Power Audio Amplifiers in vehicles
- A perfect capacitor does not heat up
- A capacitor has Capacitive Reactance (X_C) to AC signals
- $X_C = 1/(2 \pi f C)$
- The Impedance $Z_C = -j X_C$, where $j = \sqrt{-1}$
- We will discuss this further in a later slide


June 2025

How Capacitors Work

- Capacitors are made with two metal plates separated by air or other insulating (non-conductive of electricity) material
- The plates of the capacitor store charges (positive and negative), thus storing electricity
- The plates can be flat or wound around each other
- When insulating material is used, a measure of the material is called the dielectric constant
- The higher the dielectric constant, the larger the value of the capacitor
- The dielectric constant of a vacuum is 1.0
- The dielectric constant of air is (approximately) 1.0

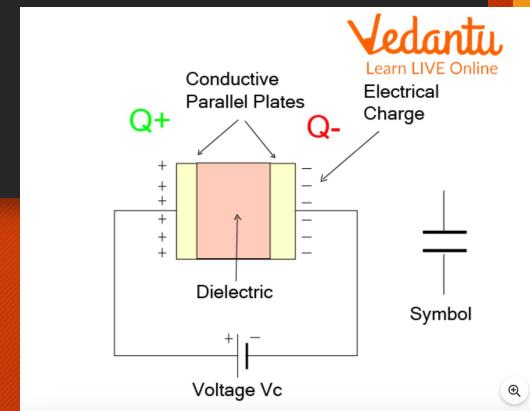

18

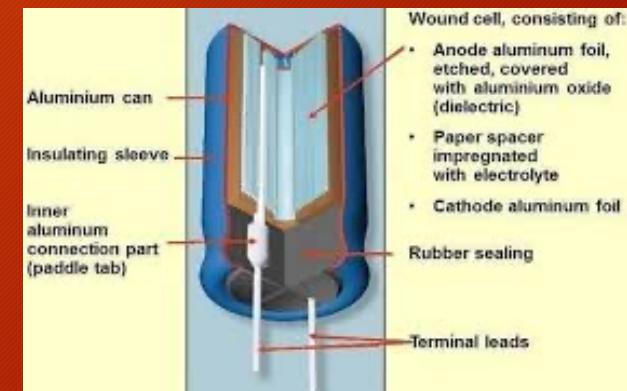

Types of Capacitors

19

- Electrolytic Capacitors are used for audio and power applications
 - They are marked with their capacitance and voltage
 - e.g., 150 uF (micro-Farads), 50 volts
 - They have a polarity: plus and minus
 - The minus lead will have a long strip next to it or a minus sign
- Ceramic Capacitors are used in radio circuits and for bypass capacitors in digital circuits
 - They are marked with their value as a number
 - e.g., 102 is 1000 uuF (Micro-Micro-Farads, or pico Farads)
 - Sometimes just 50 meaning 50 uuF (or 60 pF)
 - They have no polarity
 - Sometimes the only way to determine the value is with a capacitance meter
- Mica or Silver Mica Capacitors were found in 30s-60s Vacuum Tube radios/TVs

June 2025

Examples of Capacitors

Electrolytic



Ceramic

Air Variable Capacitors

Electrolytic

Ceramic

Electrolytic

June 2025

<https://en.wikipedia.org/wiki/Capacitor>



Inductor

21

- An inductor (L) passes both AC and DC signals
- How well an inductor passes AC signals depends on its value and the frequency of the signal
- An inductor's value is measured in Henrys
- Values are from microHenry (RF circuits) to Henrys (Power Circuits)
- A perfect inductor does not heat up
- An Inductor has Inductive (X_L) Reactance to AC Signals
- $X_L = 2 \pi f L$
- The Impedance $Z_L = +j X_C$, where $j = \sqrt{-1}$
- We will discuss this further in a later slide

How Inductors Work

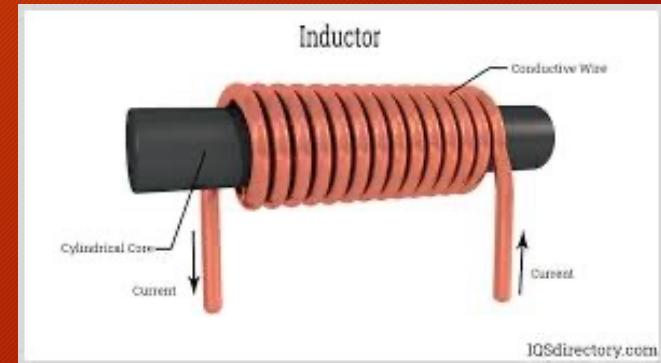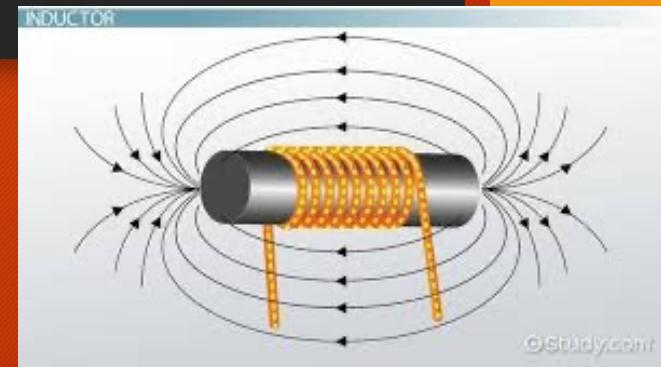
- Inductors store energy in the magnetic field created by passing electricity through wires
- Wires wound around magnetic material increase the inductance of the Inductor
- When magnetic material is used, a measure of the material is called the permeability
- The higher the permeability, the larger the value of the Inductor
- The permeability of air is 1.0



Transformers

23

- A transformer is made when two, or more, sets of windings are used on the same magnetic material
- Transformers are used to change the value of an AC signal up or down

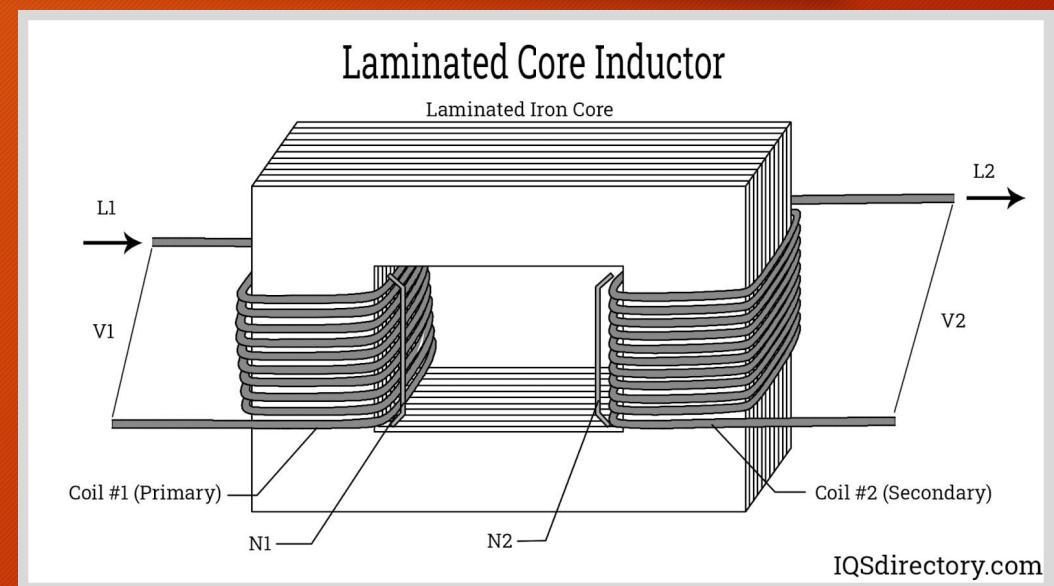

June 2025

Inductor Coding

24

- Many inductors have no coding of their size
- Some small inductors look like small resistors and use the same color code description
- You may need to use an Inductance Meter to measure them

Inductor Examples

25



June 2025

Resistors, Capacitors and Inductors in AC Circuits

26


- Resistors, Capacitors and Inductors act differently in an AC Circuit
- A simple example shows what happens when the AC signal is at only one frequency and is thus a sine wave function
- The voltage and current in a resistor are in phase
 - i.e., they rise and fall in step with each other
- The current in a capacitor is 90 degrees out of phase with the voltage
- The current in an inductor is 90 degrees out of phase with the voltage in the opposite direction to that of a capacitor
- We represent the 90 degree phase shift by using complex numbers, j ,
 - where $j = \sqrt{-1}$
 - In electric and electronic circuits, j is used instead of the math i to avoid confusing it with current, I
- See examples on the next page

June 2025

Resistor, Capacitor and Inductor in AC Circuit

27


Resistor

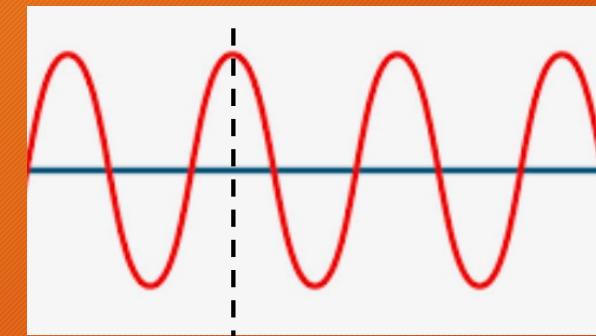

Capacitor






Inductor

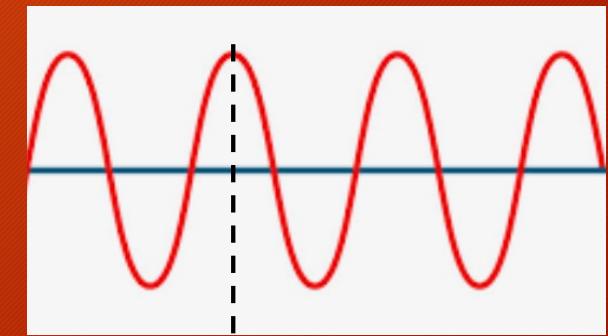

Voltage

Current

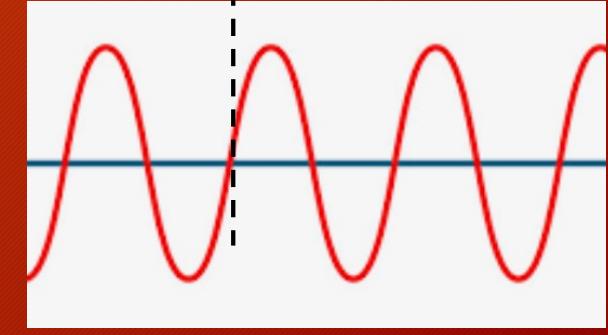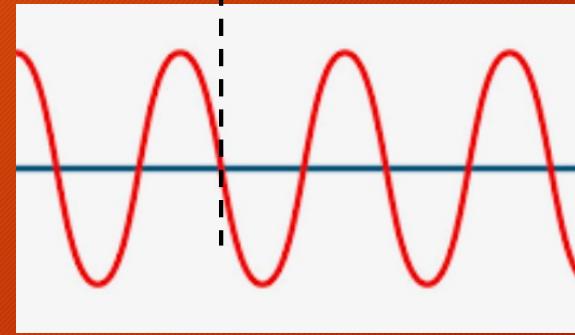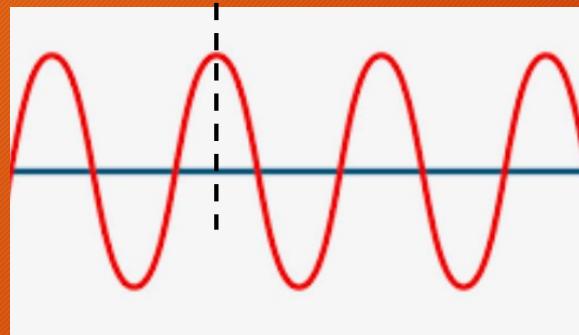

AC Series and Parallel Circuits


28

- The formulas for series and parallel circuits still apply for AC signals
- But we have to use complex math to calculate the Impedance of the circuit
- where $j = \sqrt{-1}$
- and $j \times j = -1$

Resonance

29

- A capacitor and inductor can be arranged in a Parallel circuit
- The parallel circuit is called a "Tuned Circuit"
- If you plot the impedance of the combined circuit with frequency, it peaks at a particular frequency called the resonant frequency
- The resonant frequency, f_R , is when the capacitive impedance equals the inductive impedance
- $f_R = 1 / (2\pi\sqrt{LC})$
- All inductors and capacitors have resistance
- A measure of the tuned circuit is the Q
- Q is the ratio of the impedance at resonance to the resistance of the inductor
- The higher the Q the better the tuned circuit works to filter out signals

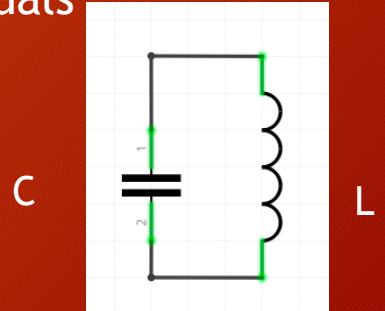

C


L

June 2025

What if the AC signal is not a sine wave

- Complex AC waves can be represented as a sum of sine waves of different frequencies
- This is expressed mathematically by the Fourier Transform
- For analyzing signals with software the Fast Fourier Transform (FFT) is used and it is often a library function in programming languages
- We use a Spectrum Analyzer to see the frequency representation of a signal

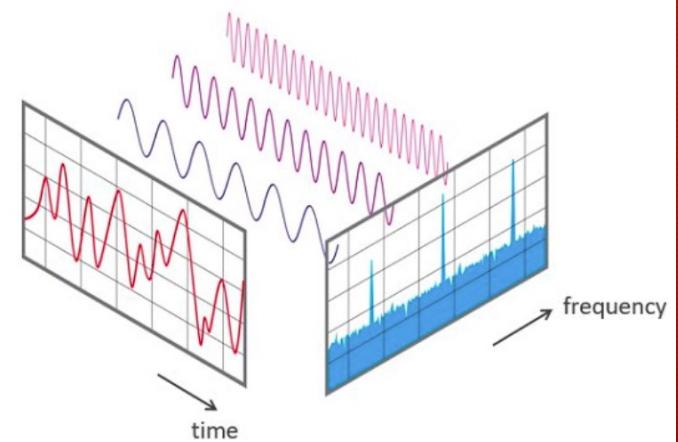Signal Processing with Fast Fourier Transform
In Python



<https://quantscience.io/newsletter/b/signal-processing-with-fast-fourier-transform>

Spectrum Analyzer


31




June 2025

Examples of Time and Frequency Domain

Time Domain

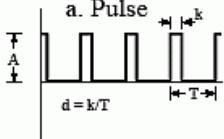

Frequency Domain


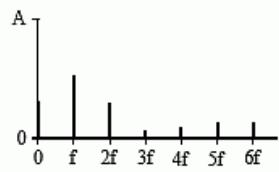


$$a_0 = Ad$$

$$a_n = \frac{2A}{n\pi} \sin(n\pi d)$$

$$b_n = 0$$



(d = 0.27 in this example)

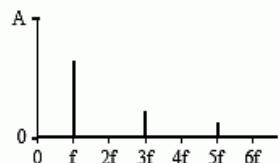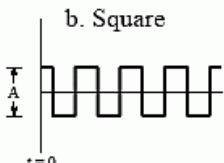

$$a_0 = 0$$

$$a_n = \frac{2A}{n\pi} \sin\left(\frac{n\pi}{2}\right)$$







(all even harmonics are zero)

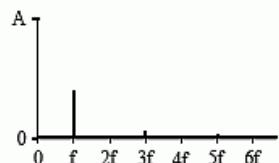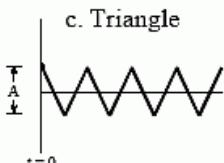

$$a_0 = 0$$

$$a_n = \frac{4A}{(n\pi)^2}$$

(all even harmonics are zero)

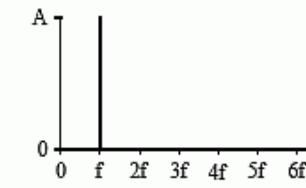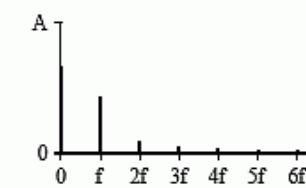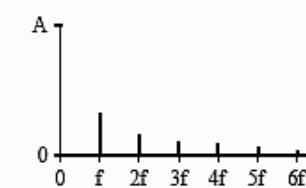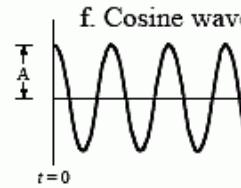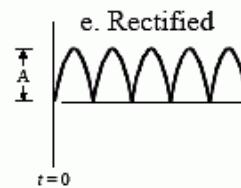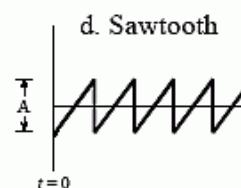

$$a_0 = 0$$

$$a_n = 0$$

$$b_n = \frac{A}{n\pi}$$

$$a_0 = 2A/\pi$$

$$a_n = \frac{-4A}{\pi(4n^2-1)}$$

$$b_n = 0$$

$$a_1 = A$$

(all other coefficients are zero)



One Final Important Point!



33

- In Electronic Circuits, by tradition:
 - Red wires are the positive connections to battery or power supply
 - Black wires are the negative and often the ground connections to the battery and power supply and to the metal chassis of the circuit
- In AC Power in houses and businesses the tradition is different
 - Black is the "Hot" wire (120 volts or 240 volts)
 - White is the neutral/return wire and is not a ground wire
 - The copper wire is the ground wire

Do not confuse the black of the power wire with the black wire of an electronic circuit.
Bad things can happen!!!!



June 2025

Questions

34

June 2025

References

35

- Radio Amateur's Handbook, ARRL, Newington CT
 - <https://www.amazon.com/ARRL-Handbook-Radio-Communications-101st/dp/1625952074>
- https://www.elenco.com/wp-content/uploads/2017/10/ECK-10_REV-O-2.pdf
- <https://www.infobooks.org/free-pdf-books/physics/electronics/>