

Questions from Last Week

1

June 2025


Questions from Last Time

2

- How are Electrolytic Capacitors constructed?
- You did not cover Back EMF from relays.

How does an Electrolytic Capacitor Work

- An electrolytic capacitor has a positive plate made of a metal that forms an insulating oxide layer through anodization.
 - The oxide layer acts as the dielectric of the capacitor.
- The electrolyte covers the surface of this oxide layer, serving as the cathode or negative plate of the capacitor.
 - The electrolyte can be solid, liquid, or gel
- A Second metal layer surrounds the electrolyte to make the electrical connection

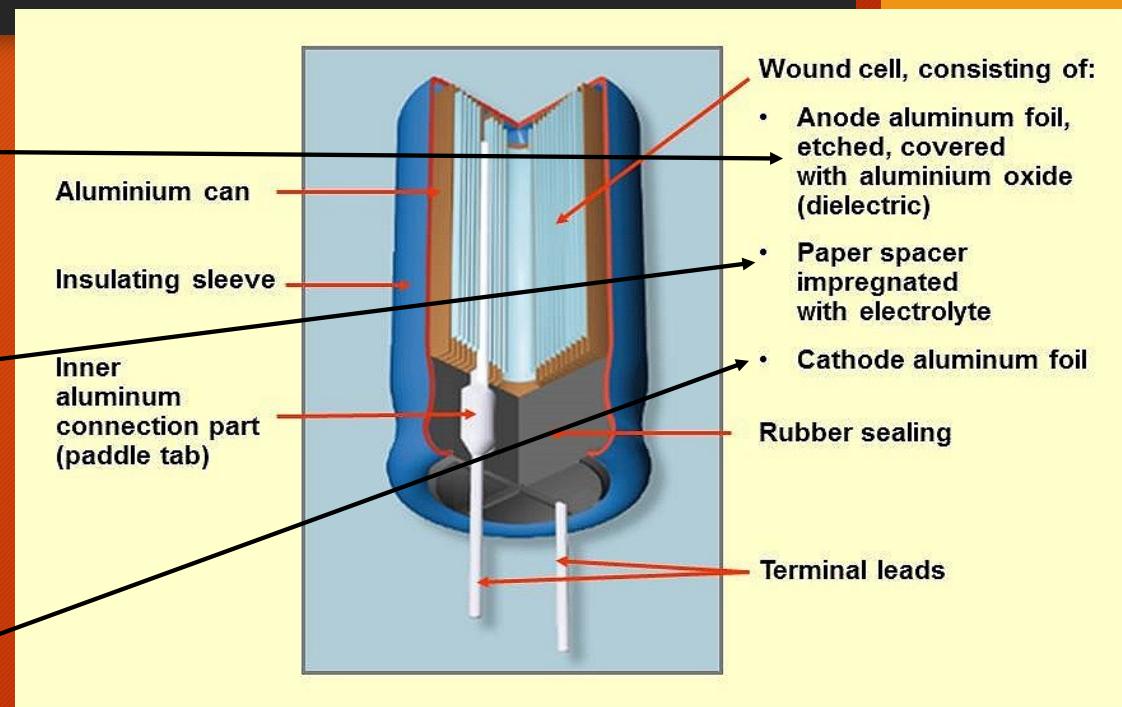


https://en.wikipedia.org/wiki/Electrolytic_capacitor

June 2025

Types of Electrolytic Capacitors

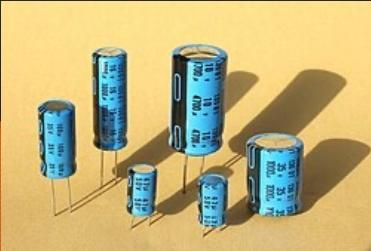- Aluminum,
 - These are the ones that leak
- Tantalum
- Niobium



Electrolytic capacitor family	Electrolyte
Aluminium-electrolytic capacitor etched foils	Non-solid, organic electrolyte, e.g. GBL , DMF , DMA ,
	Non-solid, e.g. borax, glycol
	Non-solid, water based
	Solid, polymer
	Hybrid, polymer and non-solid
Tantalum electrolytic capacitor, sintered anode	Non-solid, sulfuric acid
	Solid, manganese dioxide
	Solid, polymer
Niobium oxide-electrolytic capacitor sintered anode	Solid, manganese dioxide
	Solid, polymer

Back EMF from Inductors

- When relays are connected to electronic circuits, we must protect against the voltage spike that is caused when the relay is de-energized
- The coil of the relay stores electromagnetic energy
- When the relay is de-energized, the electromagnetic field collapses and generates a voltage of opposite polarity to the voltage that energized the relay
- This voltage is called Back Electromagnetic Force or Back EMF
- We protect against this by placing a diode across the relay in opposite polarity to the energizing voltage (See next slide)

Back EMF protection

- With the button open, transistor, Q1 has base current that results in Q2's base be zero volts and relay is off
- When the button is closed, Q1 has zero base current that results in the base of Q2 having current flow and closes the relay
- When the button is released, the diode prevents the back emf from getting greater than 0.7 volts and protects Q2

